

Circuit Simulation Modeling

Spice

TABLE OF CONTENTS

01

SPICE

02

Netlist Structure

03

Examples






Spice

❑ SPICE

(Simulation Program with Integrated Circuit Emphasis) is a widely used computer software tool for simulating and analyzing electronic circuits. It is a general-purpose circuit simulation program that allows engineers and designers to model and simulate the behavior of analog and digital circuits.

❑ Our Tool provide the following capabilities:

- Linear dc analysis
 - AC Analysis
 - Transient Analysis
- 

Netlist Structure

❑ Passive Elements

Instance Name	Component Type	From Node	To Node	Value
R	resistor	-	-	(T G M K nothing m)
C	capacitor	-	-	(f p n u m nothing)
L	inductor	-	-	(f p n u m nothing)

❑ Independent Sources

Instance Name	Component type	From Node	To Node	Type	Value
V	vsouce	-	-	dc ac	(m nothing)
I	Isouce	-	-	dc ac	(m nothing)

Netlist Structure

☐ Dependent Sources:

Instance Name	Component type	K	k'	J	J'	Type	Value
I	vccs	-	-	-	-	dc ac	(m nothing)
V	vcvs	-	-	-	-	dc ac	(m nothing)
I	cccs	-	-	-	-	dc ac	(m nothing)
V	ccvs	-	-	-	-	dc ac	(m nothing)

☐ Analysis Types:

Analysis Name	type	Analysis Name	type	Start	stop	dec	Analysis Name	type	Time step	Stop time
dcOp	dc	AC Analysis	ac	-	-	-	Transient Analysis	tran	-	-


☐ Operational Amplifier (ideal):

Analysis Name	Component type	Negative terminal	Negative terminal	Output terminal
Operational_Amplifier	opamp	-	-	-


☐ Multiple Plot:

plot	V0	V1	V2	...	V#	I_V#
------	----	----	----	-----	----	------

Examples

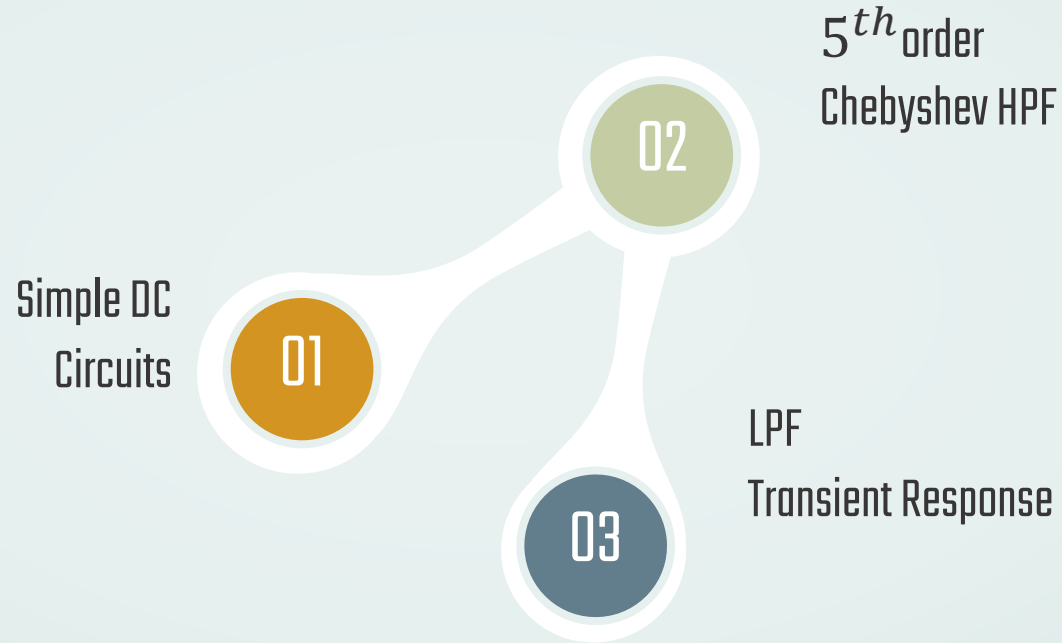

Simple DC Circuit #1

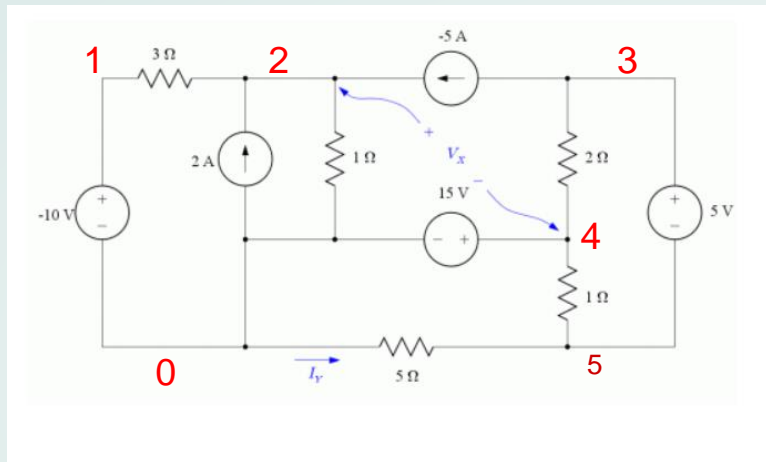

Circuit Schematic


```
// Simple DC Circuit
R1 resistor 1 2 3
R2 resistor 2 0 1
R3 resistor 3 4 2
R4 resistor 4 5 1
R5 resistor 5 0 5
V1 vsource 0 1 dc 10
V2 vsource 4 0 dc 15
V3 vsource 3 5 dc 5
I1 isource 0 2 dc 2
I2 isource 2 3 dc 5
dcOp dc
```

Netlist

```
PS D:\Python Projects\Netlist> python.exe .\main.py
V1 = [-10.]
V2 = [-4.75]
V3 = [19.70588235]
V4 = [15.]
V5 = [14.70588235]
I_V1 = [-1.75]
I_V2 = [2.05882353]
I_V3 = [2.64705882]
```

Simulation Result

Simple DC Circuit #2

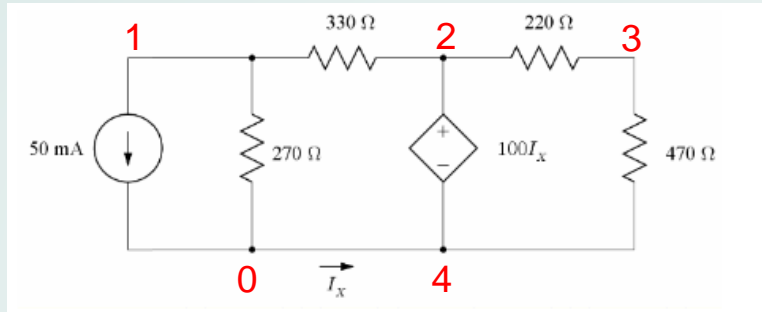

Circuit Schematic


```
// Dependent Sources  
R1 resistor 1 0 270  
R2 resistor 1 2 330  
R3 resistor 2 3 220  
R4 resistor 3 4 470  
I1 isource 1 0 dc 50m  
Vdep ccvs 2 4 0 4 dc 100  
dcOp dc
```

Netlist

```
PS D:\Python Projects\Netlist> python.exe .\main.py  
V1 = [-6.21]  
V2 = [2.7]  
V3 = [1.83913043]  
V4 = [-0.]  
I_Vdep_1 = [0.027]  
I_Vdep_2 = [-0.03091304]
```


Simulation Result

AC Analysis

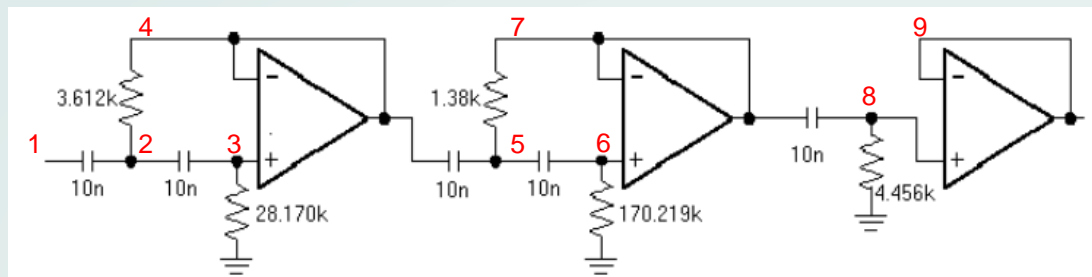

5th Order 1dB Ripple Chebyshev High Pass Filter

Circuit Schematic

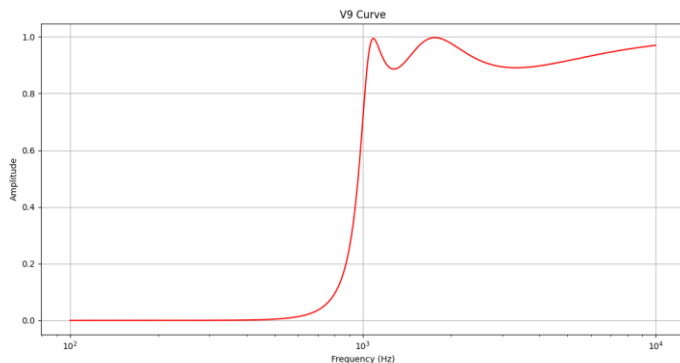

Simulation Result

```
// 5th order 1dB Ripple Chebyshev HPF
```

```
C1 capacitor 1 2 10n
```

```
C2 capacitor 2 3 10n
```

```
R1 resistor 2 4 3612
```

```
R2 resistor 3 0 28170
```

```
Opamp1 opamp 3 4 4
```

```
C3 capacitor 4 5 10n
```

```
C4 capacitor 5 6 10n
```

```
R3 resistor 5 7 1380
```

```
R4 resistor 6 0 170219
```

```
Opamp2 opamp 6 7 7
```

```
C5 capacitor 7 8 10n
```

```
R5 resistor 8 0 4456
```

```
Opamp1 opamp 8 9 9
```


```
V vsource 1 0 ac 1
```

```
ac ac 100 10K 100
```

```
plot V9
```

Netlist


Transient Analysis

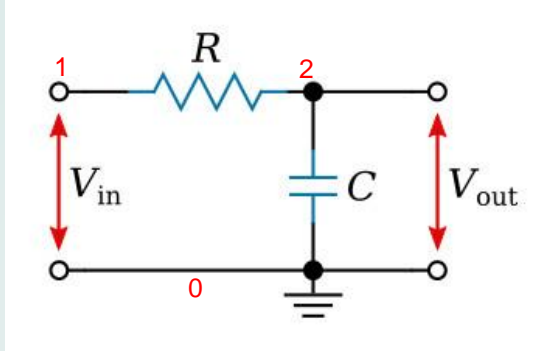

Circuit Schematic

```
// LPF  
R1 resistor 1 2 1  
C1 capacitor 2 0 1  
Vin vsource 1 0 dc 1  
tran tran 1m 10  
plot V2
```

Netlist

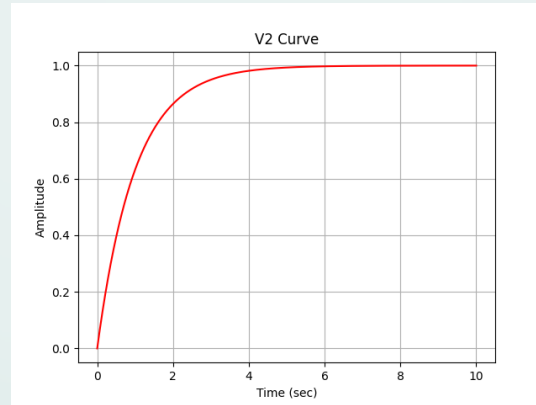

Simulation Result